1c. Battery-pack sensing: Current



- Battery pack electrical current measurements are required:
 - □ To monitor battery-pack safety
 - □ To log abuse conditions
 - □ By most state-of-charge and state-of-health algorithms
- We cannot measure electrical current directly—must convert to voltage and measure via A2D
- There are two basic methods to do so:
 - Using a resistive shunt, and
 - □ Using a Hall-effect mechanism

Dr. Gregory L. Plett University of Colorado Colorado Spring


Introduction to Battery Management Systems | BMS sensing and high-voltage control 1 of 8

Shunt current sensor



- Shunt sensor is low-value (e.g., 0.1 m Ω) high-precision resistor in series with battery pack, usually at low-voltage end
- Current computed by measuring voltage drop: $I = V_{\text{shunt}}/R_{\text{shunt}}$
- Since the shunt resistance must be small (to avoid large power losses due to $i^2R_{\rm shunt}$ heating), the voltage drop across the shunt will be small as well
- So, the voltage is usually amplified before sensing and the calculation for current is adjusted accordingly



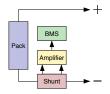

Dr. Gregory L. Plett University of Colorado Colorado Spring

Introduction to Battery Management Systems | BMS sensing and high-voltage control

1.3.5: How to sense battery-pack current in a BMS?

Shunt details



- Examining the device in more detail, note that there are four connection terminals
 - One large terminal on the top is connected to the negative terminal of the battery stack, the other to the output negative terminal of the battery pack
 - □ Pack current passes through parallel plates that form the calibrated resistance in the center of the shunt
 - □ The resistance between the two smaller screw terminals is calibrated, and the sensing leads are connected to these smaller terminals



Kelvin four-wire connection



- Connecting using these four terminals is called a Kelvin connection and enables four-wire voltage measurement
- Essentially no current is drawn by the A2D, so there is negligible voltage drop across resistance of smaller terminals: current can be calculated as stated earlier
- However, if one were to (mistakenly) connect the voltagesensing wires to the larger terminals, the voltage drop of the battery-pack current passing through the uncalibrated resistance of the terminals would significantly degrade the accuracy of the current calculation



Dr. Gregory L. Plett University of Colorado Colorado Springs

Introduction to Battery Management Systems | BMS sensing and high-voltage control 4 of 8

Shunt current-sensor comments



- Some comments on current-sensing shunts:
- Power and sense connections must be made separately
 - Shunts have no offset at zero current, so are good to avoid drift in coulomb counting (but, offset might still be introduced by amplifier or A2D)
 - Current shunts are not electrically isolated from the pack: if BMS must be isolated from pack, extra circuitry is required
 - Resistance of current shunt changes with temperature, so temperature must be measured and resistance calibrated
 - \Box Heat generated via i^2R shunt losses must be dissipated
 - □ Amplification of shunt signal is necessary—wiring must be shielded from EMI


Dr. Gregory L. Plett University of Colorado Colorado Spring

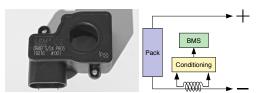1.3.5: How to sense battery-pack current in a BMS?

Hall-effect current sensing



- If a coil is wrapped around a primary current-carrying conductor, the electromagnetic field produced by the conductor induces a secondary current in the coil
- Hall-effect sensors measure this induced current to infer the primary current
- Main battery-pack current-carrying wire passes through the oval opening in the center of the sensor-no direct electrical connection is made between the sensor and the high-voltage battery pack



Dr. Gregory L. Plett University of Colorado Colorado Springs

Introduction to Battery Management Systems | BMS sensing and high-voltage control

Hall-effect current-sensor comments



- Some comments on Hall-effect sensors:
 - ☐ Hall-effect sensors are electrically isolated from pack current, so no special isolation circuitry is needed
 - □ Feedback circuitry is needed to guard against sensor magnetic hysteresis (sometimes packaged with sensor)
 - □ Even so, Hall-effect sensors suffer from offset at zero current, which changes with temperature
 - Even if "zeroed" at room temperature, will report incorrect current as they change temperature
 - As the bias plays havoc with a number of BMS algorithms, some kind of compensation is necessary



Dr. Gregory L. Plett University of Colorado Colorado Springs

Introduction to Battery Management Systems | BMS sensing and high-voltage control 7 of 8

Summary



- Battery pack electrical current must be measured to monitor safety, log abuse, and inform SOC and SOH algorithms
- Two methods may be used: either current shunt or Hall-effect sensor
- Both methods have advantages and disadvantages and both are in common use in BMS today

Dr. Gregory L. Plett University of Colorado Colorado Springs

Introduction to Battery Management Systems | BMS sensing and high-voltage control | 8 of 8